

# COL216 Lab2 : Single Cycle Processor

Poojan Shah 2022CS11594

Pritesh Mehta 2022CS11916

We briefly describe our implementation, design choices and the subsequent testing which was done for the complete single cycle datapath and control unit.


## Designing the Decode Module :

Since we are using a single cycle implementation, the decode unit does the job of the control, and is purely combinational in nature. Based on the instruction, we just need to output the control signals. Here is the RISC-V instruction format for reference :

**CORE INSTRUCTION FORMATS**

	31	27	26	25	24	20	19	15	14	12	11	7	6	0
R	funct7				rs2		rs1		funct3		rd	Opcode		
I	imm[11:0]						rs1		funct3		rd	Opcode		
S	imm[11:5]				rs2		rs1		funct3		imm[4:0]	opcode		
SB	imm[12:10:5]				rs2		rs1		funct3		imm[4:1 11]	opcode		
U	imm[31:12]										rd	opcode		
UJ	imm[20:10:1 11 19:12]										rd	opcode		

 Here is the interface for the decode module :



By observing and understanding the format of the RISC-V ISA, we can derive the following expressions for combinational logic of the control signals. We just have to differentiate opcodes/func3/func7 and utilize don't cares carefully to obtain the following :

$$Reg1 = I[19:15]$$

$$Reg2 = I[24:20]$$

$$RegW = I[11:7]$$

$$MemToReg = I[4]$$

$$RegWrite = I[4] \&\& !I[5]$$

$$MemWrite = !I[4] \&\& I[5] \&\& !I[6]$$

$$ALUSrc = ! (I[4] \&\& I[5] \mid \mid I[5] \&\& I[6] \mid \mid I[6] \&\& I[4])$$


$$ALUSel = if (I[4] \mid \mid I[6]) then 0000 else (I[4] \&\& I[5] \&\& I[30] \mid \mid I[6]) I[13:11]$$

Similarly, we implemented Imm using a MUX.


## Testing the Decode Module :

For the testing, let us use one instruction of each type :


```
add sp,t0,ra = 00128133
```

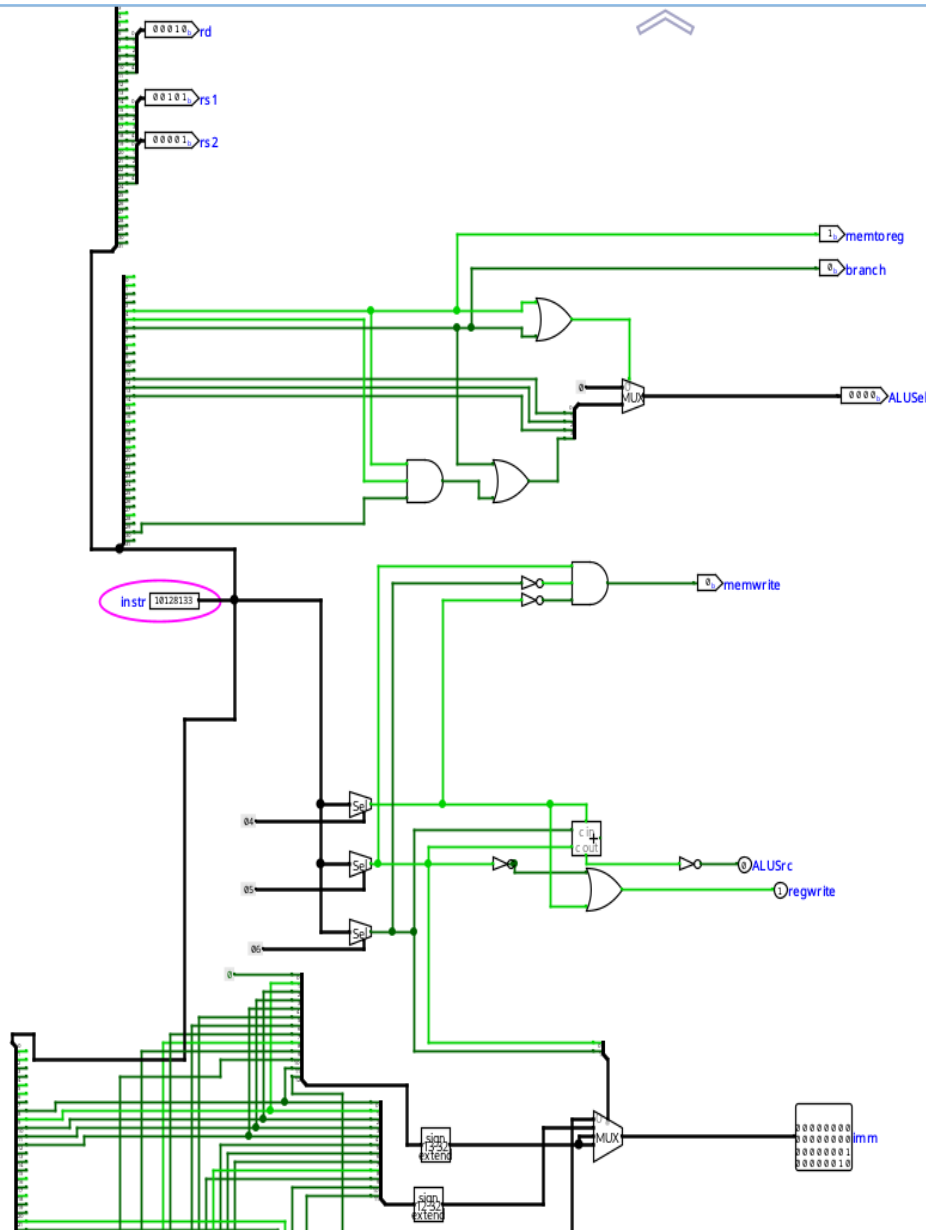


Addi sp,sp,-4 : [ffc10113](#)

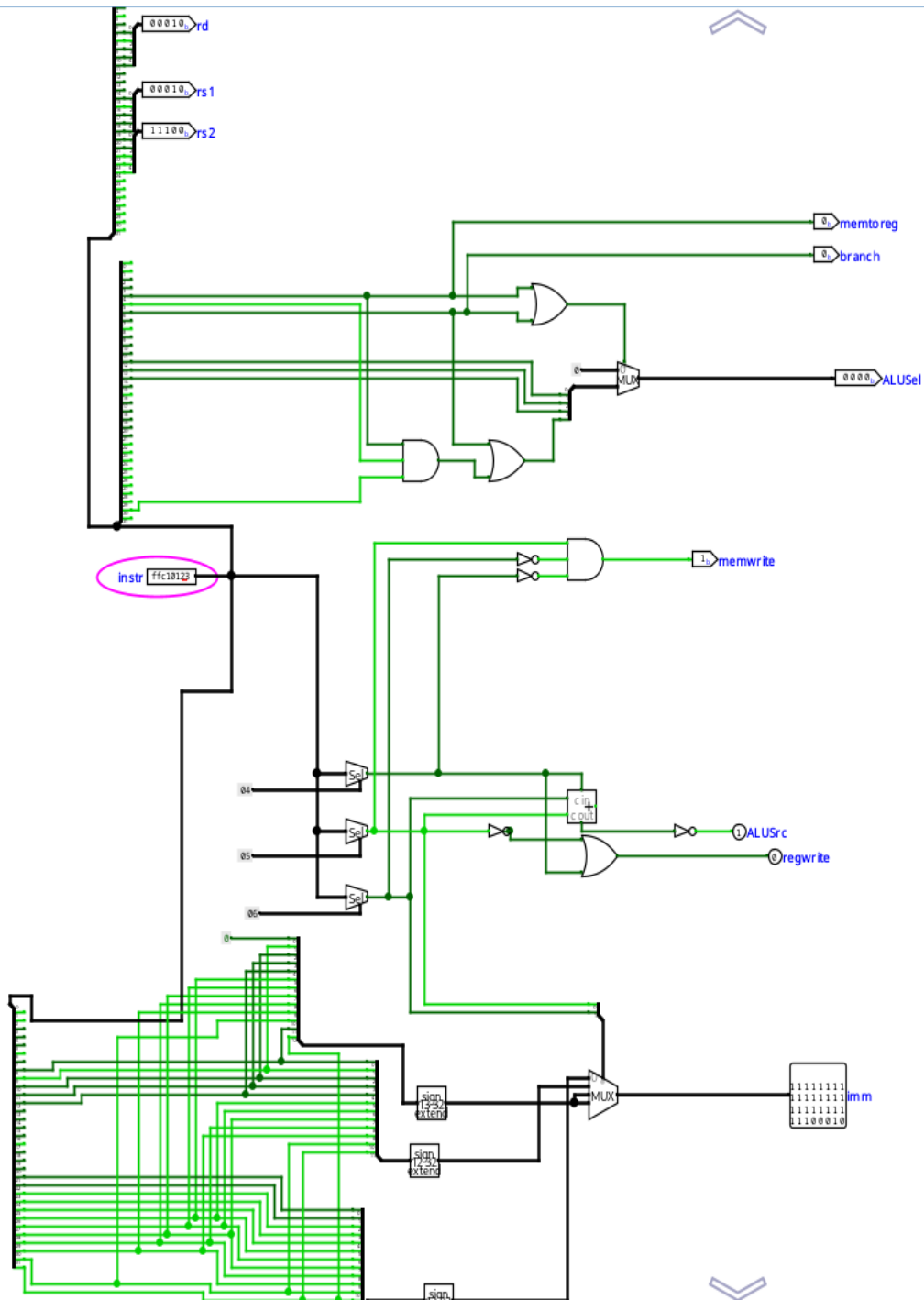


```
beq sp,ra,start : 00110063
```

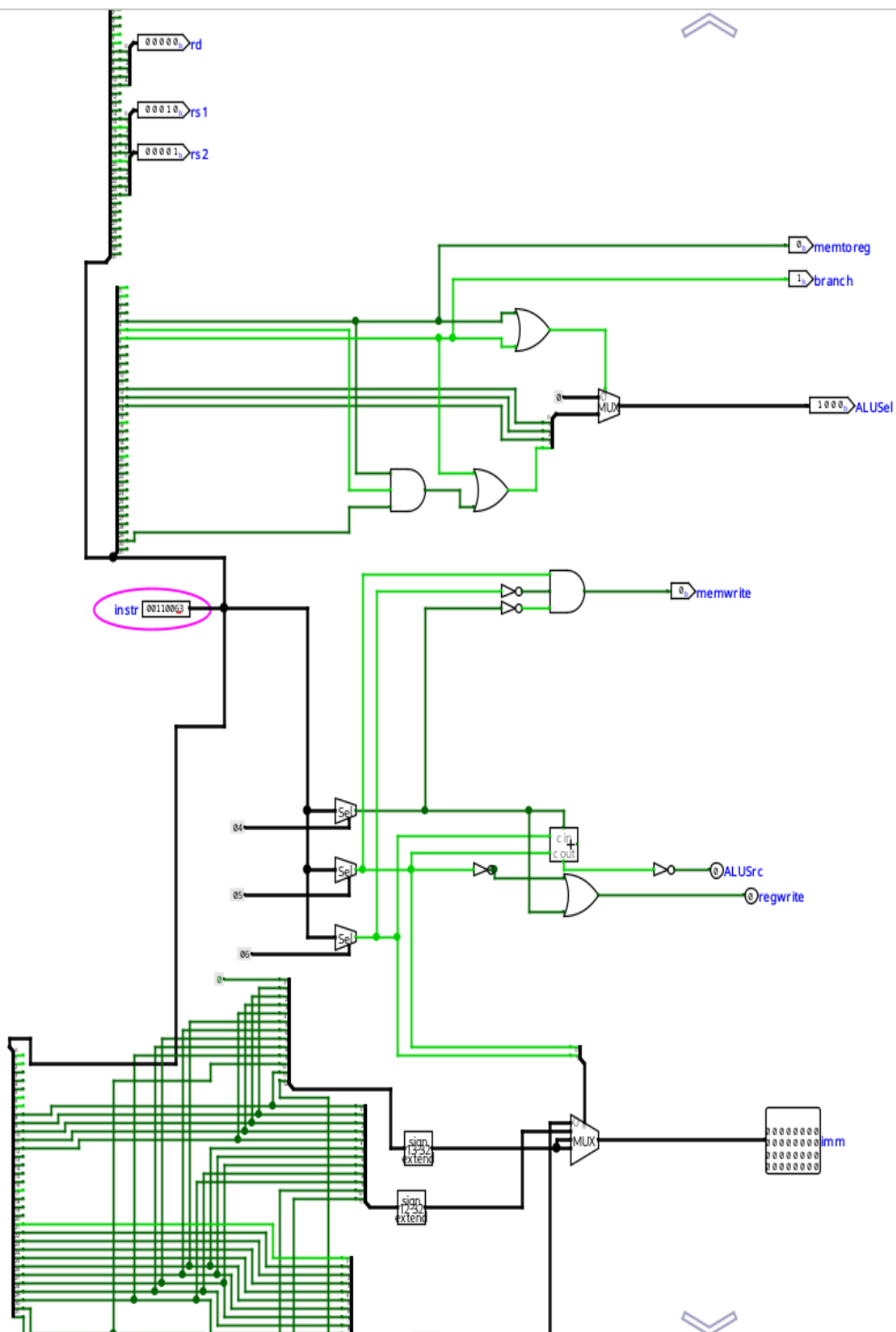

lw ra,121(sp) : 07912083

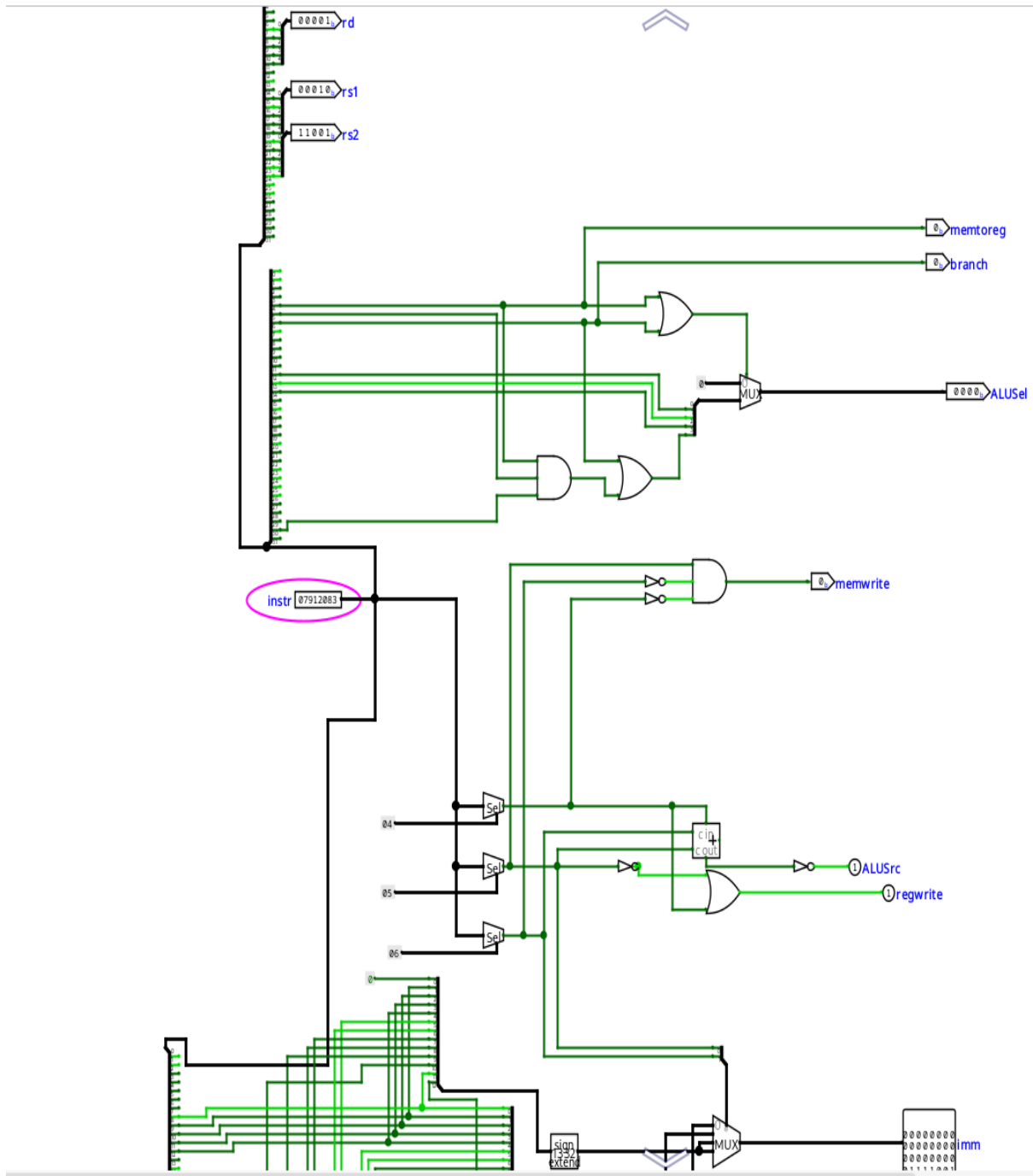


sw ra,121(sp) : 06112ca3

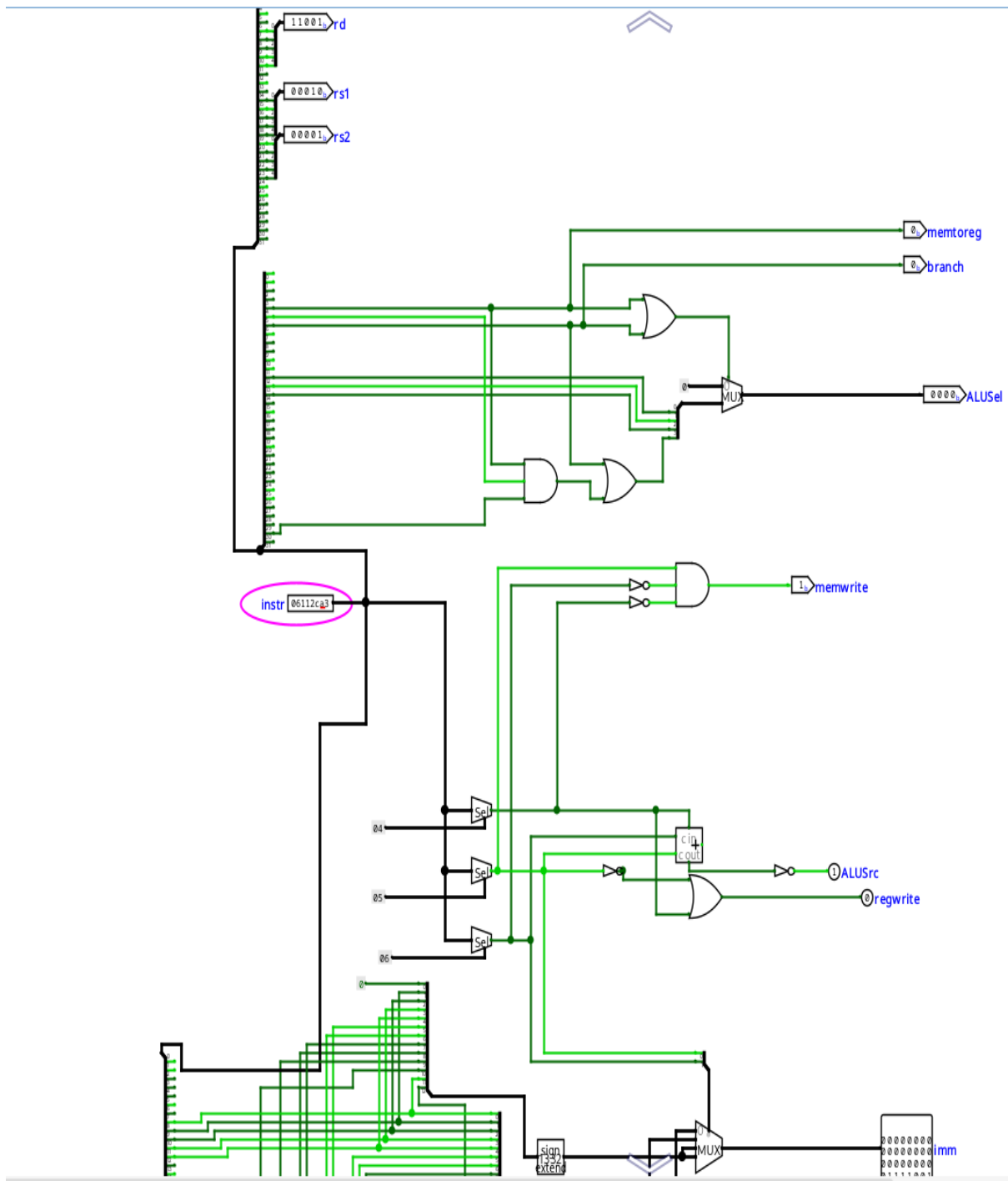


# Testing the Complete Design :

Here is the top level design :

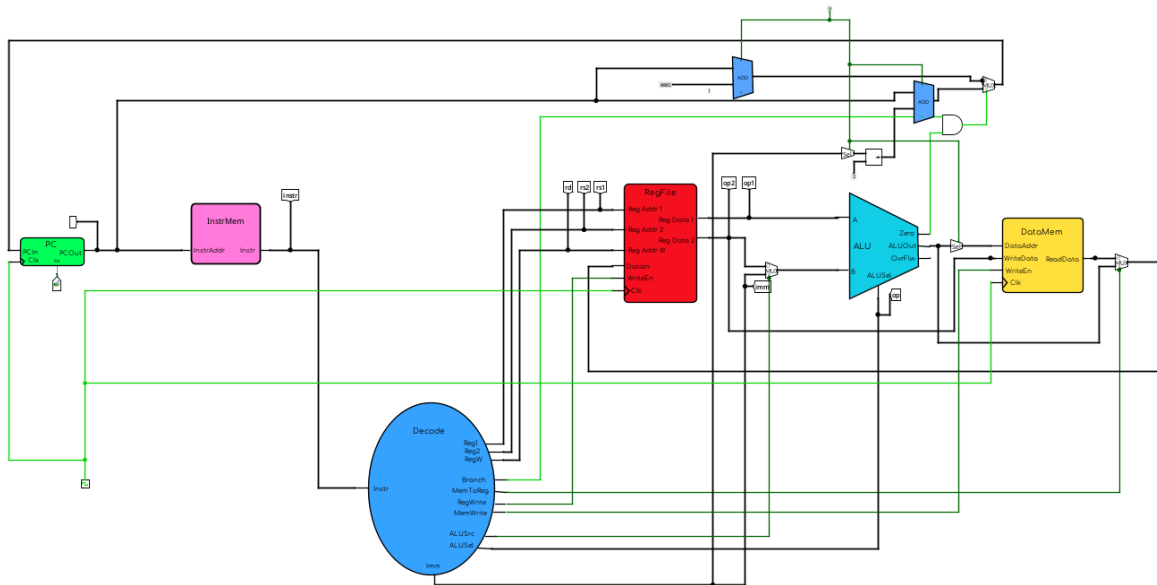

 To test the design, We need to first assemble the RISC-V code using an online assembler and then store it in the InstrMem and use the inbuilt clock ticking to observe the results. Logisim-evolution also provides VHDL-like waveforms for observation. We provide the test signals as output to the processor. For example, we show the contents of the registers at all the times :





Testing Using Simple Programs :

The following code was used to check R type Instructions :

*addi x1,x0,3*


*addi x2,x0,5*

*add x5,x1,x2*

*and x5,x1,x2*



*slt x5,x1,x2*

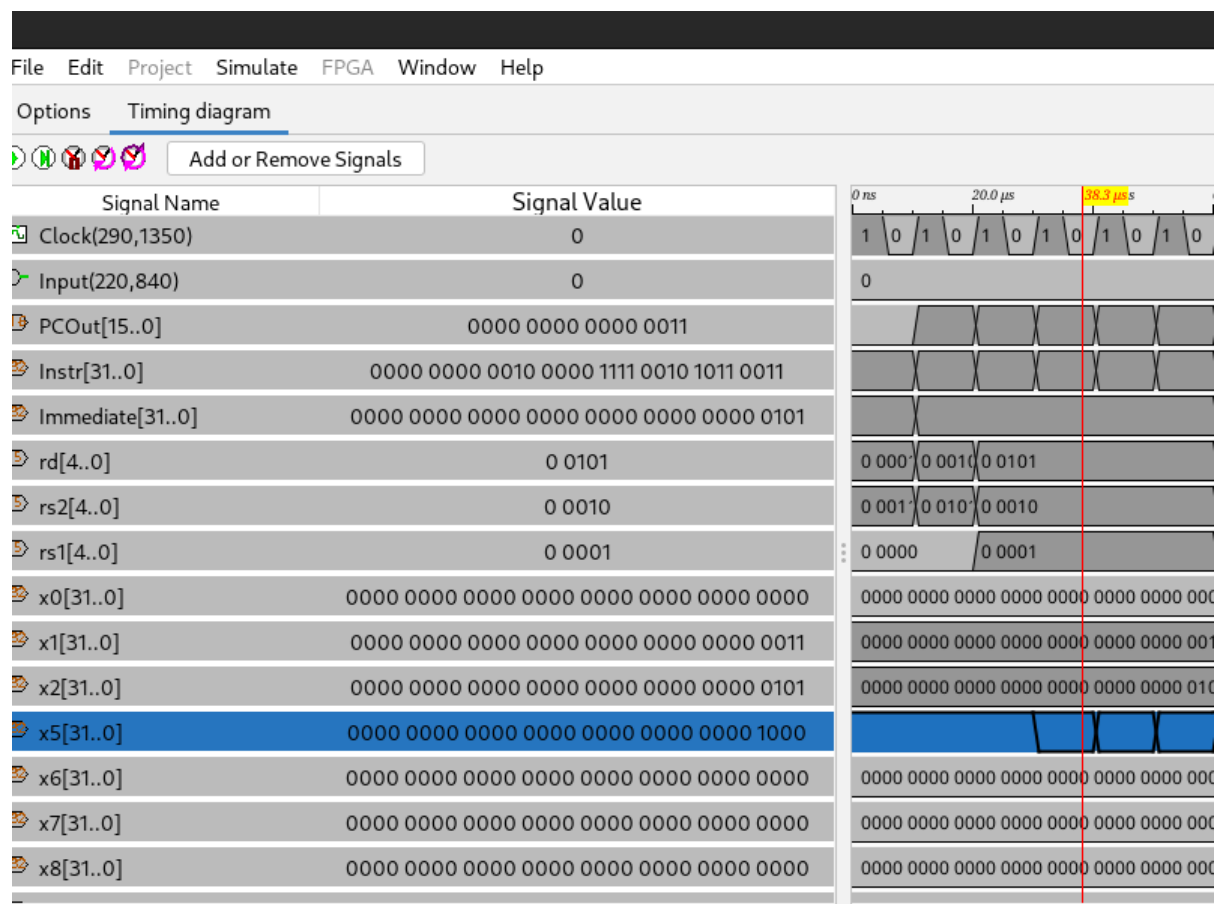Here are the timing diagram simulations for the same :





After each instruction is executed we provide the contents of the registers and the complete processor:



1.

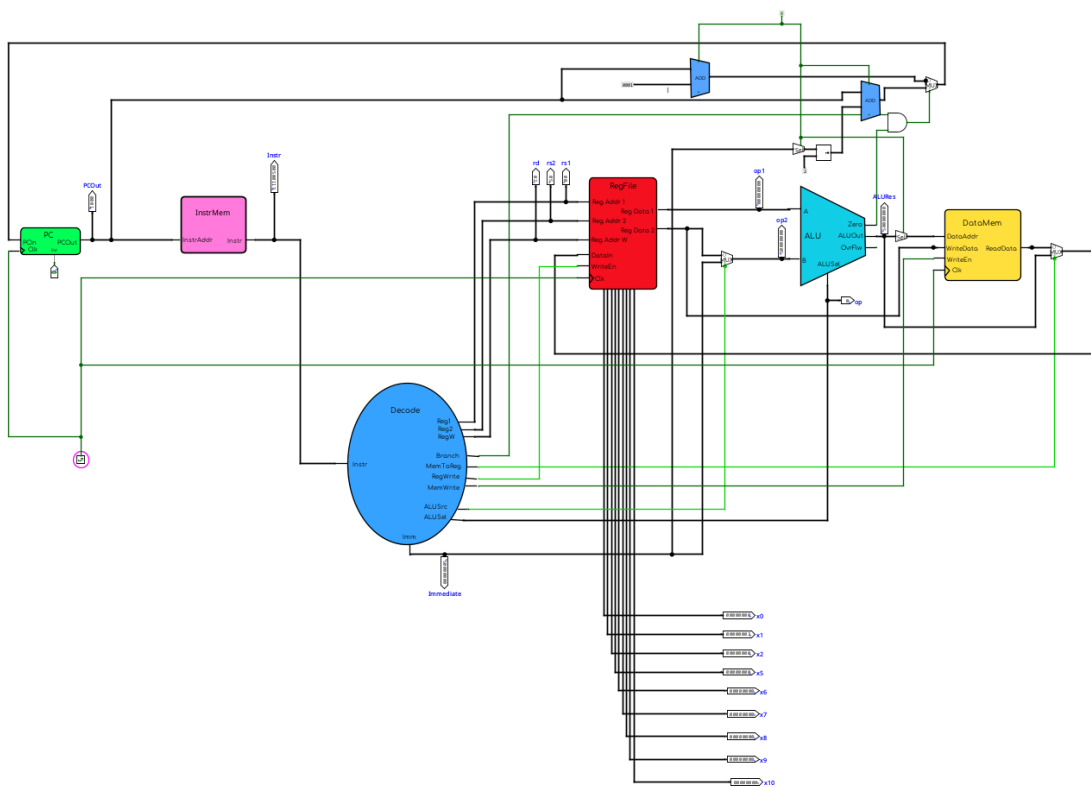 



2.

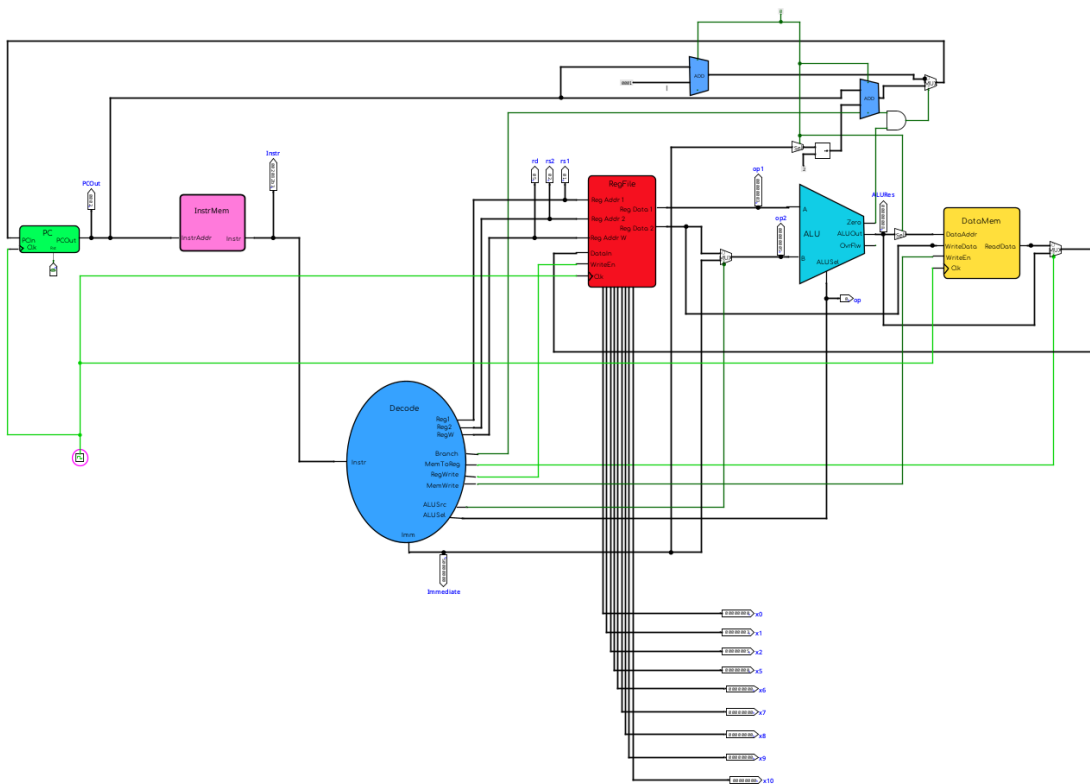 

3.

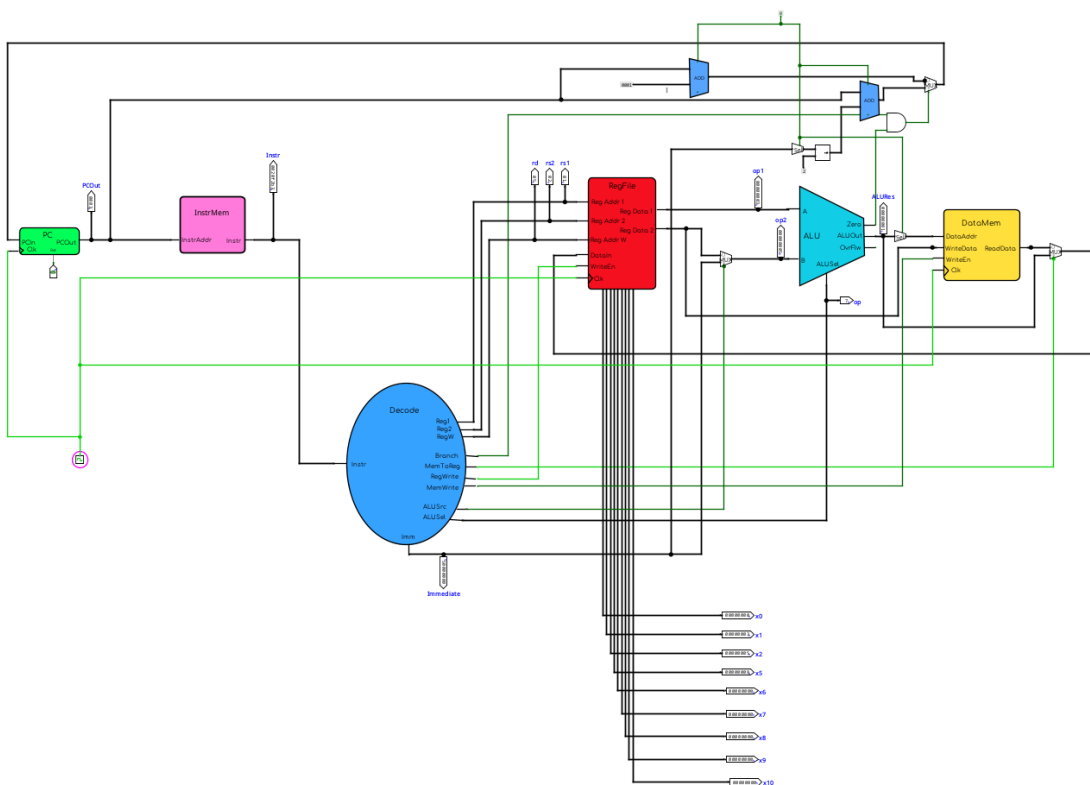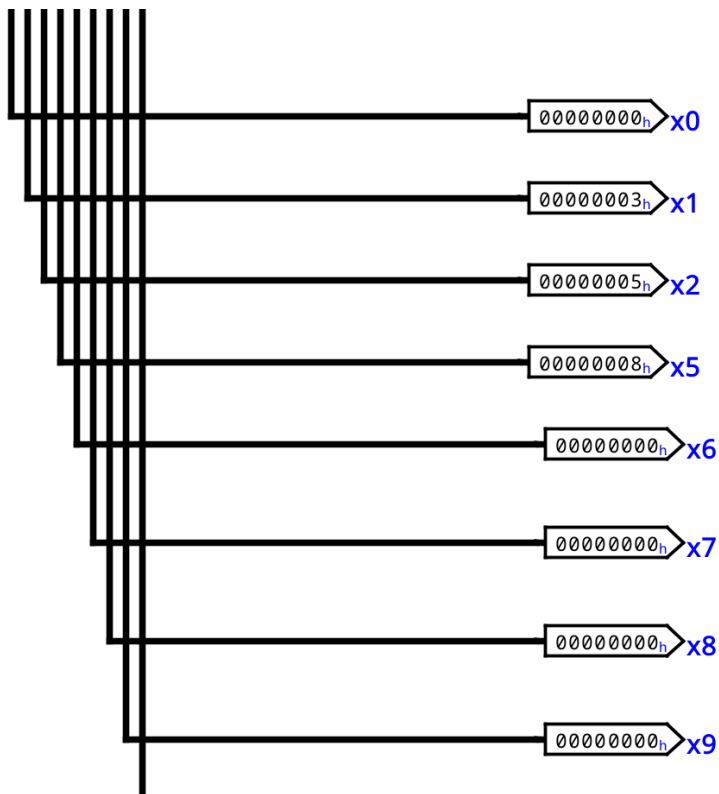

4.

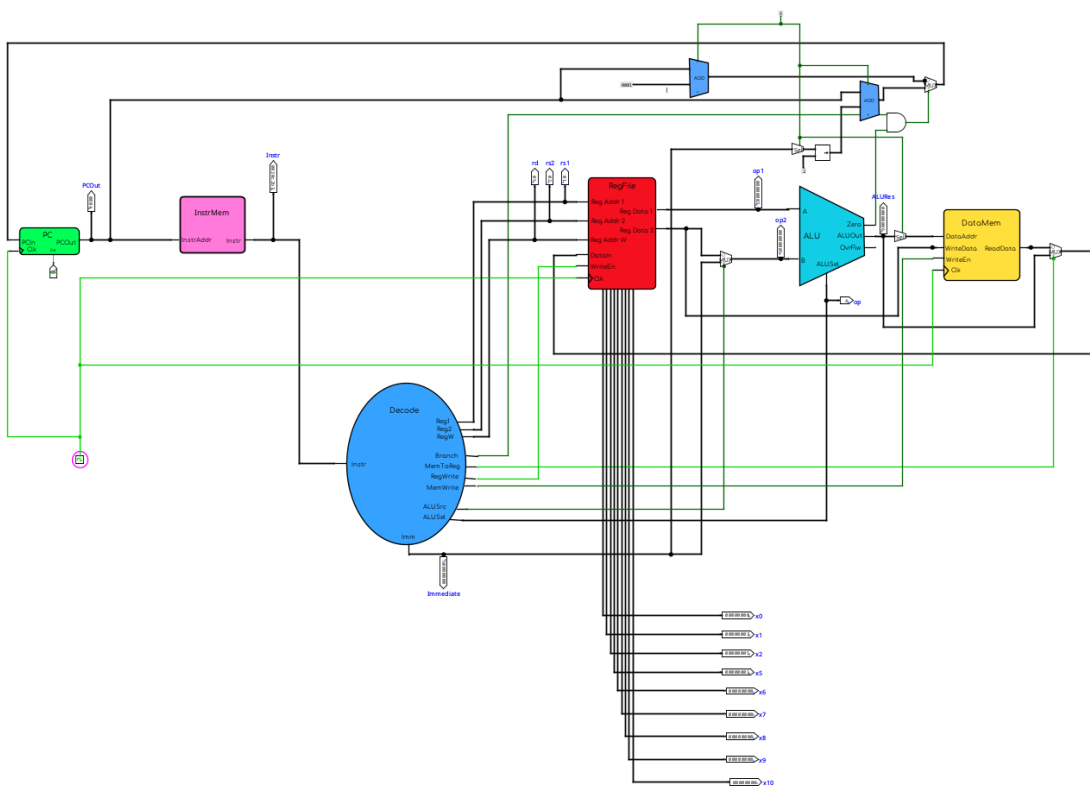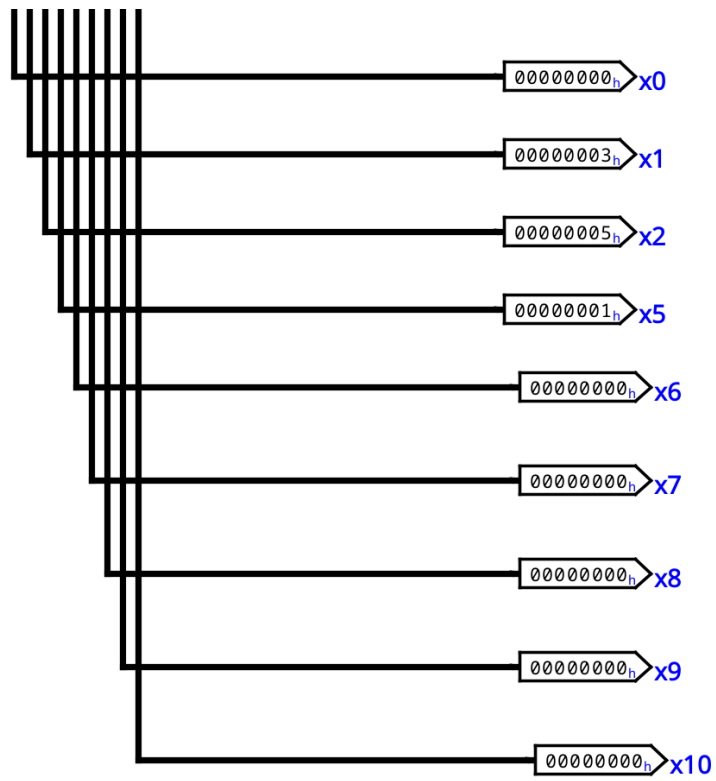

Now we test using a simple loop using branch :

```
addi x1,x0,10
```

```
addi x2,x0,0
```

```
loop:
```

```
add x2,x2,x1
```

```
addi x1,x1,-1
```


```
beq x0,x1,exit
```

```
beq x0,x0,loop
```


```
exit:
```

After the end, here are the results of the registers :

 (x2 has sum of first 10 no.s :  $55 = 37$  (hex))



HERE IS THE COMPLETE SIMULATION :

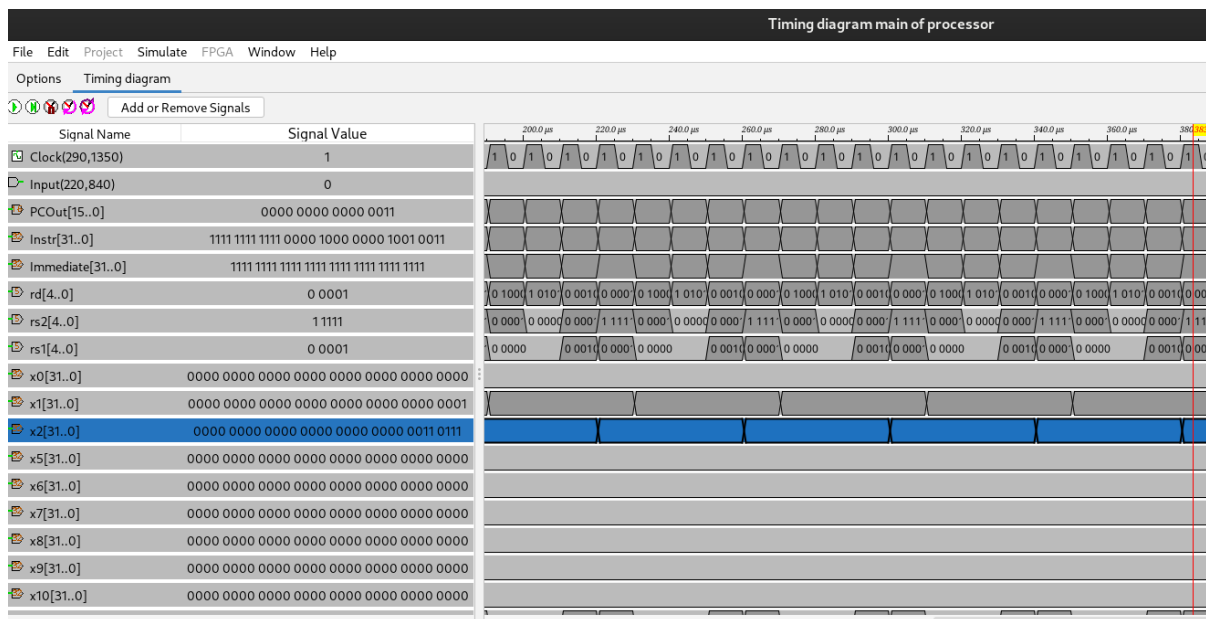


At last, we test using a small program which uses load and stores.

addi x1,x0,5


sw x1,4(x0)

lw x2 ,4(x0)

 As we can see, the loading and storing occurs correctly.



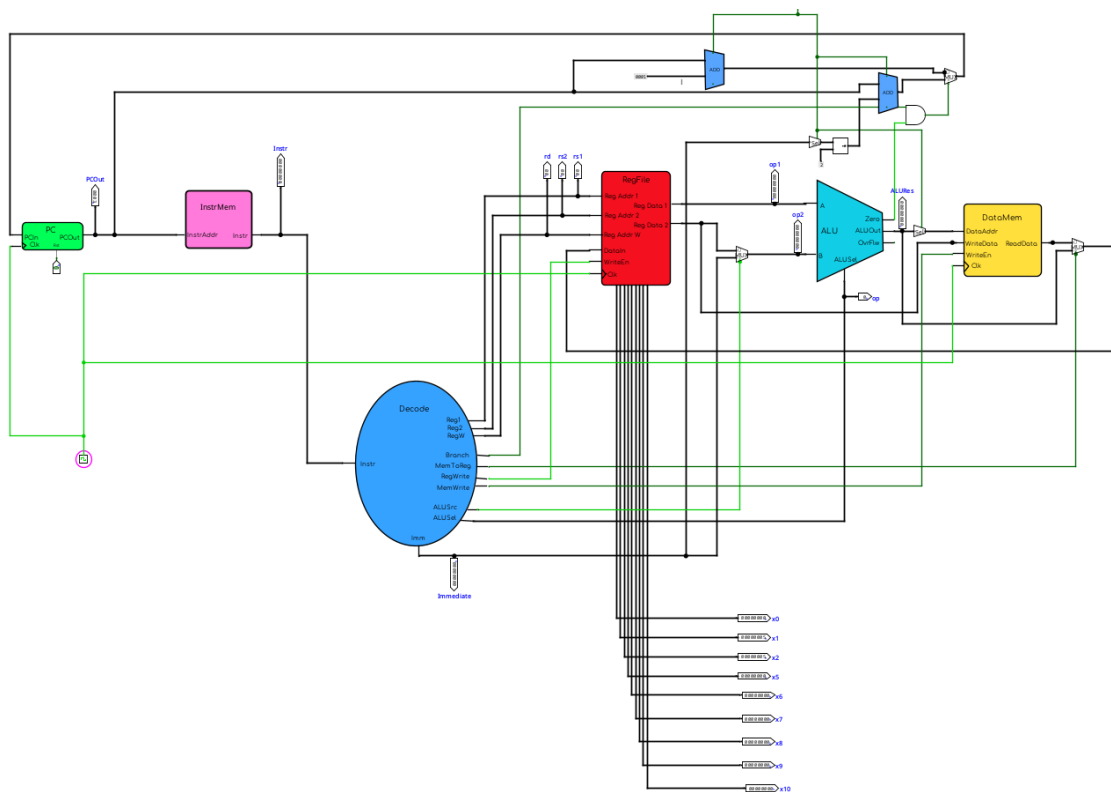Here is a picture during the load operation which highlights the datapath :



Conclusion :

We have checked all types of instructions using simple programs . We have checked that the ALU is working correctly, Branching is done correctly through testing a simple loop and that loading and storing works correctly by loading a register and then storing that value in another register.